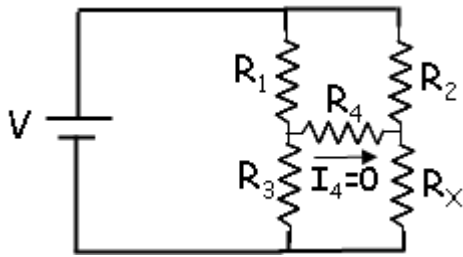


A circuit is constructed with five resistors and a battery as shown. The battery voltage is $V = 12 \text{ V}$. The values for the resistors are: $R_1 = 54 \, \Omega$, $R_2 = 132 \, \Omega$, $R_3 = 175 \, \Omega$, and $R_4 = 70 \, \Omega$. The value for R_x is unknown, but it is known that I_4 , the current that flows through resistor R_4 , is zero.



- 1) What is I_1 , the magnitude of the current that flows through the resistor R_1 ?

$$I_1 = \frac{V}{R_1 + R_3}$$

$$I = 12\text{V} / (54 \, \Omega + 175 \, \Omega) = 0.052 \text{ A}$$

- 2) What is V_2 , the magnitude of the voltage across the resistor R_2 ?

$$V_2 = V_1 = I_1 R_1 = V \frac{R_1}{R_1 + R_3}$$

$$V_2 = 12\text{V} \cdot (54 \, \Omega / (54 \, \Omega + 175 \, \Omega)) = 2.83 \text{ V}$$

- 3) What is I_2 , the magnitude of the current that flows through the resistor R_2 ?

$$I_2 = \frac{V_2}{R_2}$$

$$I_2 = 2.83\text{V} / 132 \, \Omega = 0.0214 \text{ A}$$

- 4) What is R_x , the value of the unknown resistor R_x ?

$$R_X = \frac{V_3}{I_2} = \frac{I_1 R_3}{I_1 R_1 / R_2} = R_2 \frac{R_3}{R_1}$$

$$R_x = 132\Omega(175\Omega)/54\Omega = 427.77\ \Omega$$

5) What is V_1 , the magnitude of the voltage across the resistor R_1 ?

$$V_1 = V_2$$

=2.83 V (from above)

6) If the value of the resistor R_2 were doubled, how would the value of the resistor R_3 have to change in order to keep the current through R_4 equal to zero?

Right Answer:


2

Feedback:

Your answer is correct! This circuit is called a bridge circuit. It can be used to determine the value of an unknown resistor (R_x) by varying one of the other resistors until the current between the two legs is zero. You should have found that this condition requires R_x to be determined totally by the values of the three remaining resistors.


Look at the equation for R_x , problem 4, and what happens if I_2 is varied (while assuming that the current across R_4 is still 0).

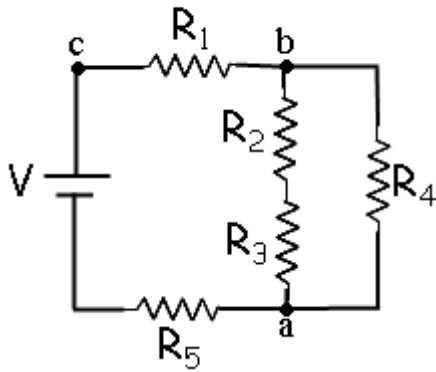A circuit is constructed with five resistors and a battery as shown. The values for the resistors are: $R_1 = 77 \, \Omega$, $R_2 = 90 \, \Omega$, $R_3 = 83 \, \Omega$, and $R_4 = 88 \, \Omega$. The battery voltage is $V = 12 \, \text{V}$.



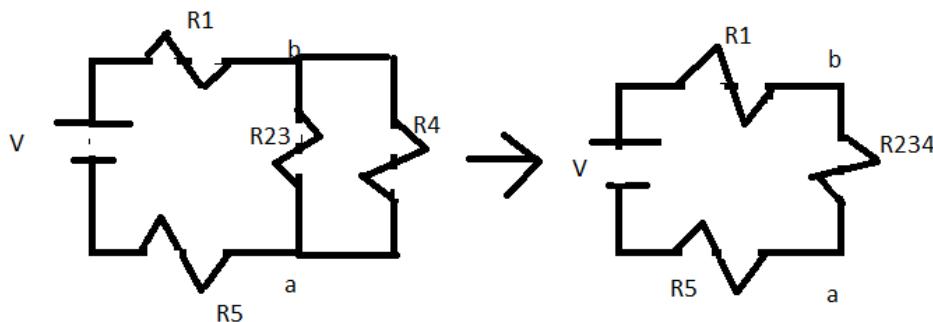- 1) What is R_{ab} , the equivalent resistance between points a and b?

$$R_{23} = R_2 + R_3 \Rightarrow R_{ab} = \frac{R_4 R_{23}}{R_4 + R_{23}} = \frac{R_4 (R_2 + R_3)}{R_4 + R_2 + R_3}$$



You try making an awesome looking circuit diagram in Paint! There is the reduction of the circuit into equivalent circuits shown by the equations above.

$$R_{234} = 88(90+83)/(88+90+83) \, \Omega = 58.33 \, \Omega$$

- 2) What is R_{ac} , the equivalent resistance between points a and c?

$$R_{ac} = R_1 + R_{ab}$$

$$R_{ac} = 77\Omega + 58.33\Omega = 135.33 \, \Omega$$

3) What is I_5 , the current that flows through resistor R_5 ?

$$R_{equiv} = R_5 + R_{ac} \Rightarrow I_5 = \frac{V}{R_{equiv}} :$$

$$R_{equiv} = 77\Omega + 135.33\Omega = 212.33\Omega$$

$$I_5 = 12V / 212.33\Omega = .056\text{ A}$$

4) What is I_2 , the current that flows through resistor R_2 ?

$$V_{ab} = V - 2V_{bc} = V - 2I_5R_5 = V - 2R_5 \frac{V}{R_5 + R_{ac}} = V \left(\frac{R_{ac} - R_5}{R_{ac} + R_5} \right)$$

$$V_{ab} = I_2(R_2 + R_3) \Rightarrow I_2 = \frac{V_{ab}}{(R_2 + R_3)} = \frac{V}{(R_2 + R_3)} \left(\frac{R_{ac} - R_5}{R_{ac} + R_5} \right)$$

$$I_2 = 12\text{ V} (135.33 - 77)\Omega / [(90 + 83)(135.33 + 77)]\Omega = .019\text{ A}$$

5) What is I_1 , the current that flows through the resistor R_1 ?

$$I_1 = I_5 \Rightarrow I_1 = \frac{V}{R_5 + R_{ac}}$$

$$I_1 = 12V / (77 + 135.33)\Omega = .056\text{ A}$$

6) What is V_4 , the voltage across resistor R_4 ?

$$V_4 = V_{ab} = V - 2V_{bc} = V \left(\frac{R_{ac} - R_5}{R_{ac} + R_5} \right)$$

Look at prob 4, you probably already calculated this.

$$V_4 = 12\text{ V} (135.33 - 77)\Omega / (135.33 + 77)\Omega = 3.296\text{ V}$$