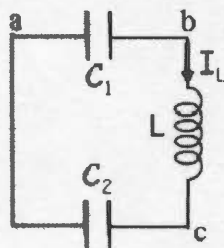


The next six questions pertain to the situation described below.



put your calculator  
in radians!

A circuit is constructed with two capacitors and an inductor as shown. The values for the capacitors are:  $C_1 = 350 \mu\text{F}$  and  $C_2 = 77 \mu\text{F}$ . The inductance is  $L = 275 \text{ mH}$ . At time  $t = 0$ , the current through the inductor has its maximum value  $I_L(0) = 200 \text{ mA}$  and it has the direction shown.

1) What is  $\omega_0$ , the resonant frequency of this circuit?

✓ 240.031481603074 radians/s

capacitors in series for this circuit

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$C = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = 63.11 \mu\text{F}$$

$$= \frac{1}{\sqrt{63.11 \times 10^{-6} \times 0.275}}$$

$$\omega_0 = 240. \text{ rad/s}$$

2) What is  $Q_1(t_1)$ , the charge on the capacitor  $C_1$  at time  $t = t_1 = 15.3 \text{ ms}$ ? The sign of  $Q_1$  is defined to be the same as the sign of the potential difference  $V_{ab} = V_a - V_b$  at time  $t = t_1$ .

✓  $-4.21861487770325 \times 10^{-4} \text{ C}$

$I, V_L, V_C, Q_C$  all oscillate at freq.  $\omega_0$ , initial conditions determine whether each has  $\sin(\omega t)$  or  $\cos(\omega t)$ .  $I = I_{\max} \cos(\omega t)$ ,  $Q_C = Q_{\max} \sin(\omega t)$  because  $\oplus$  charge is initially flowing clockwise. \* note  $Q_1 = Q_2 = Q$  series capacitors

Note that  $I = \frac{\partial Q}{\partial t}$   $I(t) = \omega Q_{\max} \cos(\omega t)$   
so  $Q_{\max} = \frac{I_{\max}}{\omega_0} = 8.33 \times 10^{-4} \text{ C}$

$$Q(t_1) = Q_{\max} \sin(\omega_0 t_1) = (8.33 \times 10^{-4}) \sin(240. \times 0.0153)$$

$$Q_1(t_1) = -4.22 \times 10^{-4} \text{ C}$$

3) What is  $V_{bc}(t_1) = V_b - V_c$ , the voltage across the inductor at time  $t_1 = 15.3 \text{ ms}$ ? Note that this voltage is a signed number.

✓ 6.68403915688049 V

~~the voltage across the inductor is not the same as the voltage across the capacitors~~  
rather

$$I(t) = 200 \text{ mA} \cos(\omega t)$$

$$|V_{bc}| = |\mathcal{E}| = L \frac{\partial I}{\partial t} = L \omega I_{\max} \sin(\omega t)$$

$$V_{bc} = -L \omega I_{\max} \sin(\omega t) \text{ for initial conditions show } (-)$$

$$V_{bc}(t_1) = -(240.) (.2) \sin(240. \times 0.0153)$$

$$= +6.68 \text{ V}$$

4) What is  $Q_{1,\max}$ , the magnitude of the maximum charge on capacitor  $C_1$ ?

$\checkmark 8.33224036548374 \times 10^{-4} \text{ C}$

found in 2)  $Q_{\max} = \frac{I_{\max}}{\omega} = \underline{8.33 \times 10^{-4} \text{ C}}$

from  $I = \frac{dQ}{dt} = \omega Q_{\max} \sin(\omega t)$

5) At time  $t = t_2$ , the magnitude of the current through the inductor has its maximum value. What are the magnitudes of  $Q_1$ , the charge on capacitor  $C_1$ , and  $V_L$ , the voltage across the inductor at this time?

1.  $Q_1 = 0$  and  $V_L = V_{\max}$
2.  $Q_1 = Q_{\max}$  and  $V_L = V_{\max}$
3.  $\checkmark Q_1 = 0$  and  $V_L = 0$
4.  $Q_1 = Q_{\max}$  and  $V_L = 0$


$I$  is maximum so  $V_L = 0$

~~$V_{L1} = V_{L2} = 0$~~

when  $V_L = 0$   $V_{C1} = V_{C2} = 0$  by Kirchhoff's Voltage loop equation

when  $V_C = 0$   $Q_C = 0$  since  $V = \frac{Q}{C}$   
so  $Q_1 = Q_2 = 0$

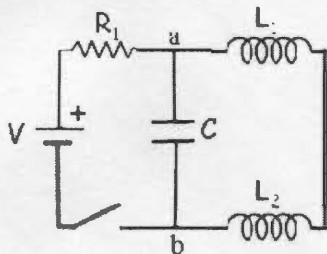The next seven questions pertain to the situation described below.



A circuit is constructed with a resistor, two inductors, one capacitor, one battery and a switch as shown. The value of the resistance is  $R_1 = 300 \Omega$ . The values for the inductances are:  $L_1 = 210 \text{ mH}$  and  $L_2 = 182 \text{ mH}$ . The capacitance is  $C = 98 \mu\text{F}$  and the battery voltage is  $V = 12 \text{ V}$ . The positive terminal of the battery is indicated with a + sign.

7) The switch has been closed for a long time when at time  $t = 0$ , the switch is opened. What is  $U_{L1}(0)$ , the magnitude of the energy stored in inductor  $L_1$  just after the switch is opened?

✓  $1.68 \times 10^{-4} \text{ J}$  before  $t=0$  ~~capacitor~~ C is uncharged, current flows in outer loop. ~~at~~  $t=0$  current remains same through inductors.

$$I = \frac{V}{R_1} = .04 \text{ A}$$

$$U_1 = \frac{1}{2} L_1 I^2 = \frac{1}{2} (.21 \text{ H}) (.04 \text{ A})^2 = 1.68 \times 10^{-4} \text{ J}$$

8) What is  $\omega_0$ , the resonant frequency of the circuit just after the switch is opened?

✓ 161.340696947366 radians/s

LC circuit

L in series add  $L = L_1 + L_2 = 392 \text{ mH}$



$$\omega_0 = \frac{1}{\sqrt{LC}} = 161. \text{ rad/s}$$

9) What is  $Q_{\text{max}}$ , the magnitude of the maximum charge on the capacitor after the switch is opened?

✓ 247.922568557201  $\mu\text{C}$

since  $I = \frac{\partial Q}{\partial t}$  and  $Q = -Q_{\text{max}} \sin(\omega t)$  (set by initial conditions)  
 $I = I_{\text{max}} \cos(\omega t)$

we see that  $I_{\text{max}} = \omega \cdot Q_{\text{max}}$

$$\text{so } Q_{\text{max}} = \frac{I_{\text{max}}}{\omega_0} = \frac{(.04 \text{ A})}{(161.3) \text{ rad/s}} = 2.48 \times 10^{-4} \text{ C} = \underline{248 \mu\text{C}}$$

10) What is  $Q(t_1)$ , the charge on the capacitor at time  $t = t_1 = 3.22$  ms.  $Q(t_1)$  is defined to be positive if  $V(a) - V(b)$  is positive.

✓ -123.083876783424  $\mu\text{C}$

$$\begin{aligned} Q(t) &= -Q_{\max} \sin(\omega t) \\ &= -248 \cancel{\mu\text{C}} \sin(161 \cdot .00322) \\ &= \underline{-123. \mu\text{C}} \end{aligned}$$

Current is flowing clockwise at  $t=0$ , so  $V_a$  is decreasing while  $V_b$  is increasing (and  $V_a = V_b = 0$  at  $t=0$ ), which determines  $-\sin(\omega t)$  factor

11) What is  $t_2$ , the first time after the switch is opened that the energy stored in the capacitor is a maximum?

✓ 9.73588827692023 ms

$V_c$ ,  $Q_c$ , and energy  $U_c$  all maximum after  $1/4$  period  
so when  $\omega_0 t = \frac{\pi}{2}$

$$\begin{aligned} t_2 &= \frac{\pi}{2\omega_0} = .00974 \text{ s} \\ &= \underline{9.74 \text{ ms}} \end{aligned}$$

12) What is the total energy stored in the inductors plus the capacitor at time  $t = t_2$ ?

✓  $3.136 \times 10^{-4} \text{ J}$

at  $t_2$  current = 0 so no energy stored in inductors.


$$\cancel{U_c} U_{\text{total}} = U_c(t_2) = \frac{1}{2} \frac{Q_{\max}^2}{C} = \underline{3.136 \times 10^{-4} \text{ J}}$$

Since there is no resistor connected to the circuit at this point, energy is conserved and is constant, so  $U = U_c + U_L$  at all times. So  $U$  also  $= \frac{1}{2} L(I_{\max})^2$



Welcome to this IE. You may navigate to any page you've seen already using the IE tab on the right.

## LC Circuit

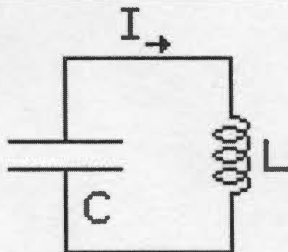

The LC circuit shown above has a capacitance  $C = 0.05 \mu\text{F}$  and inductance  $L = 420 \text{ mH}$ . Suppose that at time  $t = 0$ , the stored electric and magnetic energies are equal to one another and the instantaneous current is  $75 \text{ mA}$ . What is  $Q_{\text{max}}$ , the maximum charge that is stored on the capacitor in this situation?  $Q_{\text{max}} =$

C

Submit

Graph

Help

Right Answer:  ✓

magnetic:  $U_L = \frac{1}{2} L I^2$  > given that  $U_L = U_C$  at  $t=0$  and  $I = 75 \text{ mA}$  at  $t=0$   
 electric:  $U_C = \frac{1}{2} \frac{Q^2}{C}$

total energy is conserved since no resistor is present, so

$$U_T = U_L + U_C \quad \text{is constant}$$

$$\text{at } t=0 \quad U_T = 2 \times U_L = L I(0)^2 = .00236 \text{ J}$$

when  $Q_C = Q_{\text{max}}$ ,  $I=0$  so  $U_L=0$  and  $U_C = U_T = .00236 \text{ J}$

$$U_C = \frac{1}{2} \frac{Q_{\text{max}}^2}{C} \quad \text{at } t=0 \text{ when } Q = Q_{\text{max}}$$

$$\text{so } \frac{1}{2} \frac{Q_{\text{max}}^2}{C} = U_T$$


$$Q_{\text{max}} = \sqrt{2CU_T} = \sqrt{2CL I(0)^2} \\ = 1.54 \times 10^{-5} \text{ C}$$



Welcome to this IE. You may navigate to any page you've seen already using the IE tab on the right.
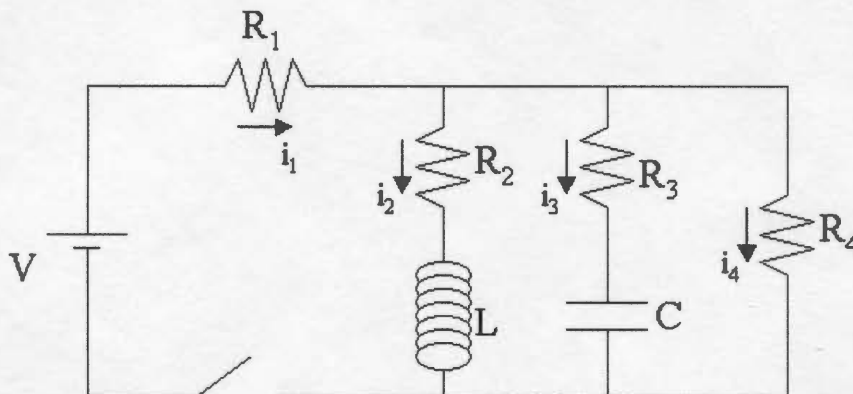
### Stored Energy in LCR Circuit

Four resistors ( $R_1 = 60 \text{ Ohms}$ ,  $R_2 = 220 \text{ Ohms}$ ,  $R_3 = 330 \text{ Ohms}$ , and  $R_4 = 480 \text{ Ohms}$ ), an ideal inductor ( $L = 8 \text{ mH}$ ), and a capacitor ( $C = 250 \text{ microF}$ ) are connected to a battery ( $V = 9 \text{ V}$ ) through a switch as shown in the figure below.



The switch has been open for a long time before it is closed at  $t = 0$ . What is  $U_{\text{stored}}$ , the total stored energy in the circuit elements (not including the battery) a long time after the switch is closed?  $U_{\text{stored}} =$

,00519

J Submit

Graph

Help

Right Answer: 0.005186056 J ✓

Only  $L$  and  $C$  store energy.


$$U_L = \frac{1}{2} L I^2$$

$$U_C = \frac{1}{2} C V^2$$

At  $t = \infty$  capacitor is fully charged and prevents current through it.  
inductor allows current to flow like a wire and has no Voltage

$$V_L = 0$$

So circuit looks like:

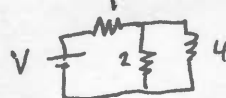

we need to find:  $I_L = I_2$

$$V_C = V_{R2} = V_{R4}$$

because it is in a parallel branch.

solving this circuit gives  $I_2 = 0.0293 \text{ A}$

$$V_{R2} = V_{R4} = 6.44 \text{ V}$$

$$\text{so } U = \frac{1}{2} L I_L^2 + \frac{1}{2} C V_C^2$$

$$= \frac{1}{2} [(0.008)(0.0293)^2 + (250 \times 10^{-6})(6.44)^2]$$

$$U = 0.00519 \text{ J}$$