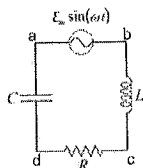


The next six questions pertain to the situation described below.



A circuit is constructed with an AC generator, a resistor, capacitor and inductor as shown. The generator voltage varies in time as  $\varepsilon = V_a - V_b = \varepsilon_m \sin \omega t$ , where  $\varepsilon_m = 120$  V and  $\omega = 215$  radians/second. The inductance  $L = 250$  mH. The values for the capacitance  $C$  and the resistance  $R$  are unknown. What is known is that the current in the circuit leads the voltage across the generator by  $\phi = 38$  degrees and the average power delivered to the circuit by the generator is  $P_{avg} = 132$  W.

Known

$\varepsilon_m$

$\omega$

$L$

$\phi = -38^\circ$

$P_{avg}$

unknown

$C$

$R$

Useful equations

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$I_m = \varepsilon_m / Z$$

$$I(t) = I_m \sin(\omega t - \phi)$$

$$\tan \phi = \frac{\omega L - 1/\omega C}{R}$$

$$P_{avg} = \frac{1}{2} I_m^2 R$$

1) What is  $I_{max}$ , the amplitude of the current oscillations in the circuit?

✓ 2.79183885123368 A

Note that  $Z = \sqrt{R^2 + (R \tan \phi)^2} = R \sec \phi$  which can be further rearranged

to give  ~~$Z = \frac{R}{\cos \phi}$~~   $Z = \frac{R}{\cos \phi}$

so  $I_{max} = \frac{\varepsilon_m \cos \phi}{R}$

~~to solve for R then substitute here to get~~  $P_{avg} = \frac{1}{2} I_m^2 R$

$P_{avg} = \frac{1}{2} \varepsilon_m I_m \cos \phi$   
(actually just from here)

$$I_m = \frac{2 P_{avg}}{\varepsilon_m \cos \phi}$$

$$= \frac{2(132)}{(120) \cos(38^\circ)}$$

$$I_m = 2.79 \text{ A}$$

2) What is  $R$ , the value of the resistance of the circuit?

✓ 33.8706268015442  $\Omega$

Now use  $P_{avg} = \frac{1}{2} I_m^2 R$

$$R = \frac{2 P_{avg}}{I_m^2} = \frac{2(132)}{(2.79)^2} = 33.9 \Omega$$

3) What is  $C$ , the value of the capacitance of the circuit?

✓ 57.9854361775539  $\mu\text{F}$

Use  $\tan \phi = \frac{\omega L - 1/\omega C}{R}$  (or  $I_m = \varepsilon_m / Z$ )

$$\rightarrow R \tan \phi = \omega L - \frac{1}{\omega C}$$

$$\frac{1}{\omega C} = \omega L - R \tan \phi$$

$$\frac{1}{C} = \omega^2 L - \omega R \tan \phi = (215)^2 (250) - (215)(33.9) \tan(38^\circ) = 17,246$$

$$C = \frac{1}{17,246} = 58.0 \times 10^{-6} \text{ F}$$

4) The value of  $\omega$  is now changed, keeping all other circuit parameters constant, until resonance is reached. How was  $\omega$  changed?

1. ✓  $\omega$  was increased

2.  $\omega$  was decreased

since current leads voltage,  $\phi$  is negative and

$X_C > X_L$  to reach resonance ( $X_L = X_C$ )

$\frac{1}{\omega C} > \omega L$   $\omega$  must increase.

5) What is the average power delivered to the circuit when it is in resonance?

✓ 212.57356830703 W

at resonance  $Z = R$

~~(R does not change)~~  
(R does not change)


$$I_m = \frac{E_m}{R}$$

$$\text{so } P_{\text{avg}} = \frac{1}{2} I_m^2 R = \frac{1}{2} \frac{E_m^2}{R}$$

$$P_{\text{avg}} = \frac{1}{2} \frac{E_m^2}{R} = \frac{1}{2} \frac{(120)^2}{(33.9)}$$

$$\underline{P_{\text{avg}} = 212.6 \text{ W}}$$

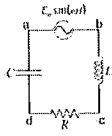The next seven questions pertain to the situation described below.



A circuit is constructed with an AC generator, a resistor, capacitor and inductor as shown. The generator voltage varies in time as  $\varepsilon = V_a - V_b = \varepsilon_m \sin \omega t$ , where  $\varepsilon_m = 24 \text{ V}$  and  $\omega = 150 \text{ radians/second}$ . At this frequency, the circuit is in resonance with the maximum value of the current  $I_{\max} = 0.63 \text{ A}$ . The capacitance  $C = 182 \mu\text{F}$ . The values for the resistance  $R$  and the inductance  $L$  are unknown.

useful equations (at resonance)

known	unknown
$\varepsilon_m$	$R$
$\omega$	$L$
$I_m$	
$C$	
$\phi = 0$ (resonance)	

$$I_m = \frac{\varepsilon_m}{R}$$

$$U_{\max} = \frac{1}{2} L I_m^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$

$$X_L = X_C \rightarrow \frac{1}{\omega C} = \omega L$$

$$\Delta U = P_{\text{avg}} \cdot T$$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$T = 1 \text{ period (in seconds)}$$

$$P_{\text{avg}} = \frac{1}{2} I_m^2 R$$

$$T = \frac{2\pi}{\omega}$$

$$P_{\text{avg}} = \frac{1}{2} \varepsilon_m I_m$$

$$Q = \frac{U_{\max}}{\Delta U} (2\pi)$$

7) What is  $L$ , the value of the inductance of the circuit?

✓ 244.200244200244 mH

$$\begin{aligned} \text{from } X_L &= X_C \\ L &= \frac{1}{\omega^2 C} = \frac{1}{(150^2)(182 \times 10^{-6})} \\ L &= .244 \text{ H} = 244 \text{ mH} \end{aligned}$$

8) What is  $U_{\max, C}$ , the value of the maximum energy stored in the capacitor during one cycle?

✓ 0.0484615384615384 J

Energy oscillates between capacitor and inductor, max energies in each are equal

~~$$U_{\max} = \frac{1}{2} L I_m^2$$~~

$$U_{\max} = \frac{1}{2} L I_m^2 = \frac{1}{2} (244) (.63)^2$$

$$U_{\max} = .0485 \text{ J}$$

9) What is  $\Delta U$ , the total energy dissipated in the circuit in one cycle?

✓ 0.316672272 J

$$\begin{aligned} P_{\text{avg}} &= \frac{1}{2} \varepsilon_m I_m & T &= \frac{2\pi}{\omega} \\ \Delta U &= P_{\text{avg}} \left( \frac{2\pi}{\omega} \right) & &= \pi \frac{\varepsilon_m I_m}{\omega} \end{aligned}$$

$$\Delta U = \frac{\pi (24) (.63)}{(150)} = .317 \text{ J}$$

10) What is Q, the quality factor of this circuit?

✓ 0.96153846153846

$$Q = \frac{U_{\max}}{\Delta U} \times 2\pi$$

$$Q = 2\pi \frac{(0.0485)}{(0.317)} = \underline{0.962}$$

11) What is R, the value of the resistance of the circuit?

✓ 38.0952380952381  $\Omega$

$$R = \frac{E_m}{I_m} = \frac{2.4}{0.63} = \underline{38.1 \Omega}$$

12) Suppose now the value of the capacitance in the circuit is doubled ( $C' = 2C$ ) and the inductance is changed appropriately to keep the circuit in resonance at angular frequency  $\omega = 150$  radians/s while the generator voltage and resistance are kept constant. How does Q, the quality factor of the circuit, change, if at all?

1. Q increases
2. Q stays the same
3. ✓ Q decreases

At resonance,  $X_L = X_C$  ~~so~~  $\omega L = \frac{1}{\omega C}$   
so if C increases, L must decrease to maintain resonance.

~~Thus  $U_{\max}$  will~~

Since R does not change,  $I_{\max}$  will not change, so  $P_{\text{avg}}$  also will not change.


So  $U_{\max} = \frac{1}{2} L I_{\max}^2$  will decrease.

$\Delta U = P_{\text{avg}} \cdot \frac{2\pi}{\omega}$  will not change.

thus  $Q = 2\pi \frac{U_{\max}}{\Delta U}$  must decrease as result.



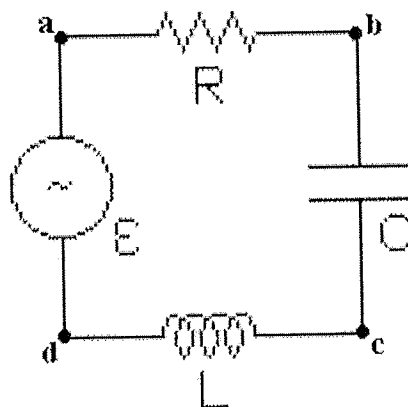Welcome to this IE. You may navigate to any page you've seen already using the IE tab on the right.  
AC Circuit 2



A series RLC circuit ( $L = 340 \times 10^{-3} \text{ H}$ ,  $C = 25 \times 10^{-6} \text{ F}$ , and  $R = 280 \text{ ohms}$ ) has an AC generator with amplitude  $\epsilon_{\text{max}} = 120 \text{ V}$  and unknown frequency  $f$ .

At time  $t = 0$ , the following voltages are measured:

$$V_{ad} = V_a - V_d = +120 \text{ V},$$

$$V_{bc} = V_b - V_c = -10.1 \text{ V}, \text{ and}$$

$$V_{cd} = V_c - V_d = +60.6 \text{ V}.$$

What is  $t_{\text{imax}}$ , the first time after  $t = 0$  that the current in the circuit attains its maximum value?  $t_{\text{imax}} =$

seconds Submit Graph

$$\star \sin(-x) = -\sin x$$

Help

Right Answer: 0.0008417383 seconds ✓

Since  $\Delta V_{ad} = 120 \text{ V}$  at  $t=0$

generator  $E = E_m \cos(\omega t)$

and  ~~$E = E_m \sin(\omega t)$~~

$$I(t) = I_m \cos(\omega t - \phi)$$

thus we need to find  $\omega$  and  $\phi$

We know also  $V_c = +X_c I_m \sin(\omega t - \phi)$  (lags current  $90^\circ$ )

$V_L = +X_L I_m \sin(\omega t - \phi)$  (leads current  $90^\circ$ )

Note that  $\frac{|V_c|}{|V_L|} = \frac{X_c}{X_L}$  is constant

$$\text{so } \frac{X_c}{X_L} = \frac{1}{\omega^2 LC} = \frac{|\Delta V_{bc}|}{|\Delta V_{cd}|}$$

$$\text{so } \omega = \sqrt{\frac{V_{cd}}{V_{bc}(LC)}} = 840 \text{ rad/s}$$

now can calculate  $\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R} \rightarrow \phi = 40.3^\circ$

$$t_{\text{imax}} = \frac{\phi}{\omega} = 0.000839 \text{ s}$$

remember  
remember to ~~convert~~  
use both in  
radians (or degrees)